

Abstract

In this lab, we continue to build on the robot's motor functionality. In Part A, we built a DC Motor Driver. This addition permits for forward and reverse rotation of the wheels. In Part B, we created a simple Speed Control circuit. These new parts allow for reliable control of the robot's speed and direction. This is essential in order for the robot to move from place to place in a precise and useful way.

Part A

DC Motor Driver Circuit

Building on the Speed Sensor from Lab 2, two DC Motor Driver circuits were built. Resistors R_{B1} and R_{B2} were calculated and then tested. This part of the circuit has the following expected parameters:

- $V_{BE1,4} \approx 0.8[V]$
- $\beta \approx 200$
- $I_{DC} \leq 1[A]$
- $R_M = 2[\Omega]$
- $V_{CC} = 10[V]$
- $R_{B1} = R_{B2} = R_B$

This lab also builds on previous findings:

- $k = 0.927$
- $f_{enc_{max}} = 1.214[kHz]$
- $J = 2.61 * 10^{-3}$
- $t_{on} = \frac{3}{4f_{enc_{max}}}$

1 Constructing DC Motor Circuit

Using the proto board supplied, the BJTs were placed onto the board and connections were soldered such that the connections matched the provided schematic for the motor driver circuit.

2 Finding R_B

2.1 R_B by hand

The specifications for R_B are simple; $|I_{DC}| < 1[A]$ if $V_{DC\ Supply} = 10[V]$. Also, $R_{B1} = R_{B2} = R_B$. The outputs from the driver, DC_1 and DC_2 , should have a total of $|1[A]|$ through the terminals if the wheels are locked. When the wheels are locked, the DC Motor from previous labs acts like a plain old $2[\Omega]$ resistor.

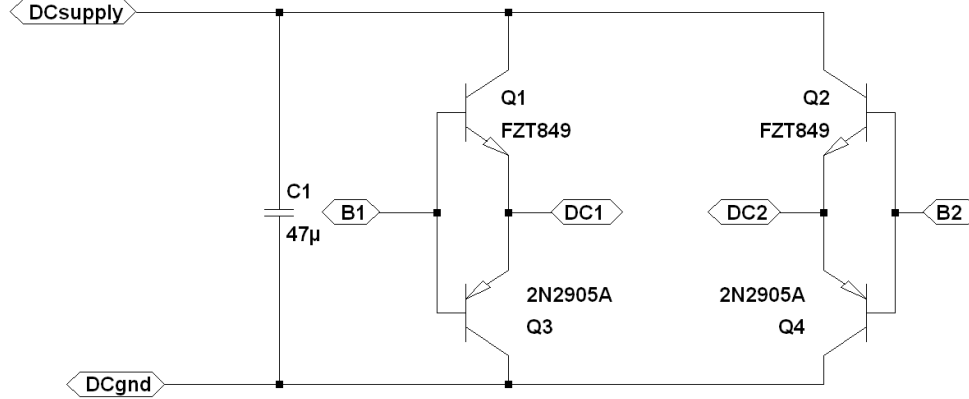


Figure 1: Complete Motor Driver Circuit

From Figure 1, it can be observed that only half of the BJT transistors are in action for a given direction (the other two BJTs are in cutoff mode). Therefore, a simplification can be made, which is shown in Figure 2. Since the mode of the two transistors is in active mode, yet another simplification can be made using dependent sources, shown in Figure 3. At this point, solving for R_B is much more straightforward:

$$V_{DC1} - V_{DC2} \leq 2[V] \quad (1)$$

$$i_B = \frac{1[A]}{(\beta + 1)} \approx 4.98[mA] \quad (2)$$

$$\beta i_B + \frac{V_{CC} - V_{BE} - V_{DC1}}{R_B} = \frac{V_{DC1} - V_{DC2}}{R_M} \quad (3)$$

$$\frac{V_{DC1} - V_{DC2}}{R_M} \leq 1[A] \quad (4)$$

$$\text{Assuming } V_{DC1} = 6[V], V_{DC2} = 4[V] \quad (5)$$

$$R_B = \frac{V_{CC} - V_{BE} - V_{DC1}}{i_B} = \frac{(10 - 0.8 - 6)[V]}{4.98[mA]} = 642[\Omega] \quad (6)$$

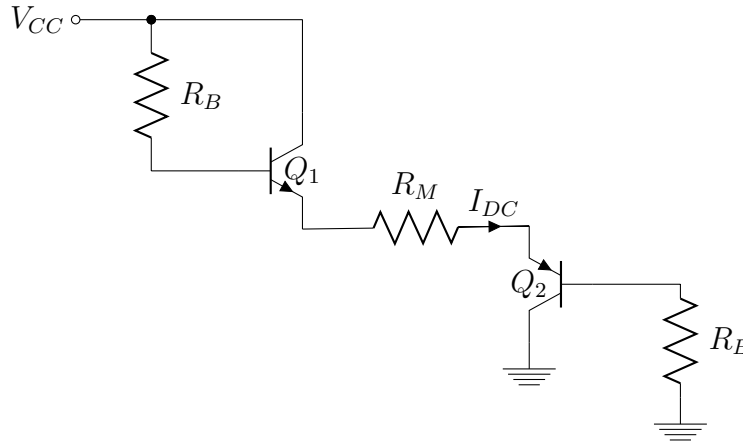


Figure 2: Simplified Model of Circuit

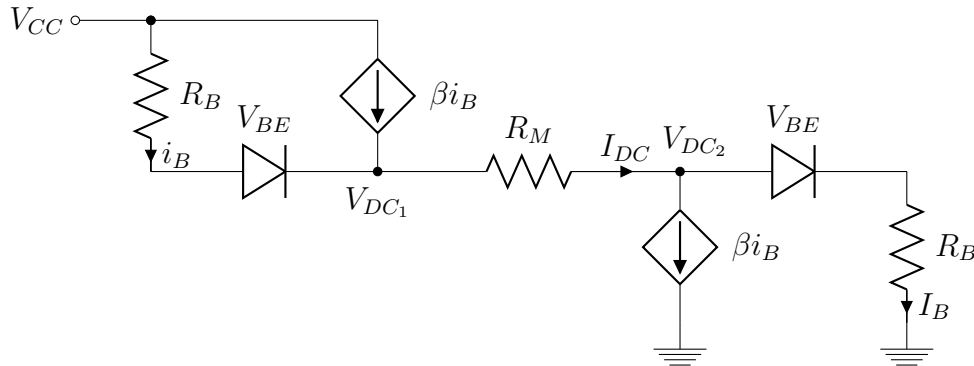


Figure 3: Further Simplified Model of Circuit

2.2 R_B by simulations

Using LTSpice, the circuit found in Figure 1 was built and then tested to see if it in fact would provide the required 1 Amp across the loading terminals. The test circuit is shown below in Figure 4. Note that X_1 is the circuit in Figure 1. Using the calculated R_B , the current through R_M was found to be 853[mA]. The voltage V_{DC1} was found to be 6.7[V] and V_{DC2} was found to be 5V. Their difference was 1.7[V]. While not ideal, this setup fulfills the required functionality. From this model, the power dissipated by the transistors can be calculated using Equation (7).

$$P[W] = (V_C - V_E)I_{DC} \approx 2.81[W] \quad (7)$$

From this expression, up to about 3 Watts of power will course through the BJTs, which is why heat sinks are used to prevent the transistors from breaking down after extensive operation.

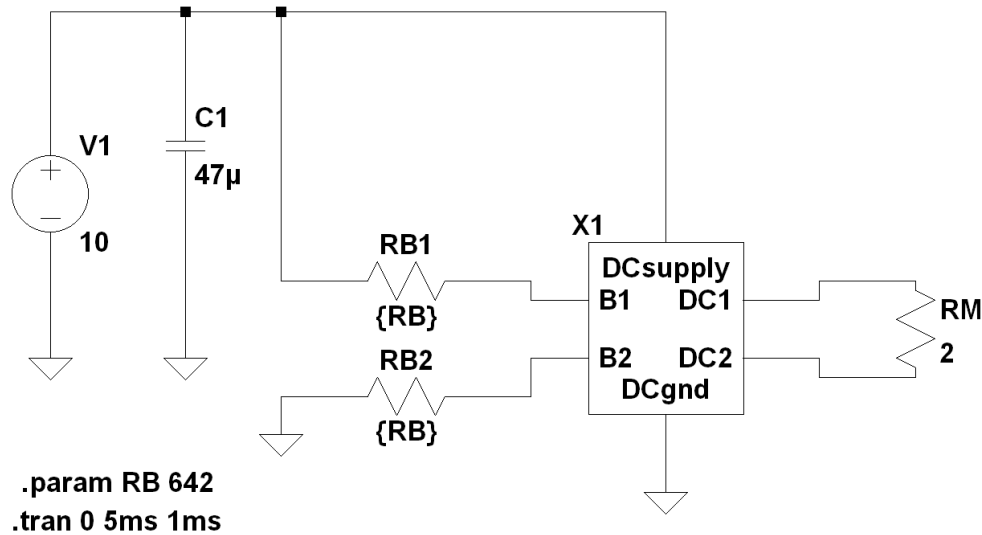


Figure 4: Motor Driver Circuit Test

2.3 R_B by experiment

Using the actual board, the same values were measured by holding the wheel in place and taking measurements. The resistor used was a pair of $642[\Omega]$ resistors.

- Locked; Clockwise configuration: $I_{DC} = 880[mA]$
- Locked; Counter-Clockwise configuration: $I_{DC} = 870[mA]$
- Either Direction Free-Rolling; $I_{DC} = 150[mA]$; Speed is $962[Hz] = 7.87[rot/s]$

Some adjustments to R_B were made throughout the experiment, but the most accurate and reliable found was the original $642[\Omega]$ resistors calculated in previous sections.

Part B

Closed-Loop Motor Driver Circuit

In this part of the lab, we constructed and tested the complete speed control circuit for a single wheel. The overall schematic for the speed control unit is shown below as Figure 5. This circuit is a feedback circuit, and can be diagrammed as such in Figure 6.

Of the parts in Figure 6, we have already built the Speed Sensor and the Driver/Motor units. The remaining part is the integral compensator, which serves the important role of improving steady-state error characteristics. This is done by adding a pole at the origin of the complex plane.

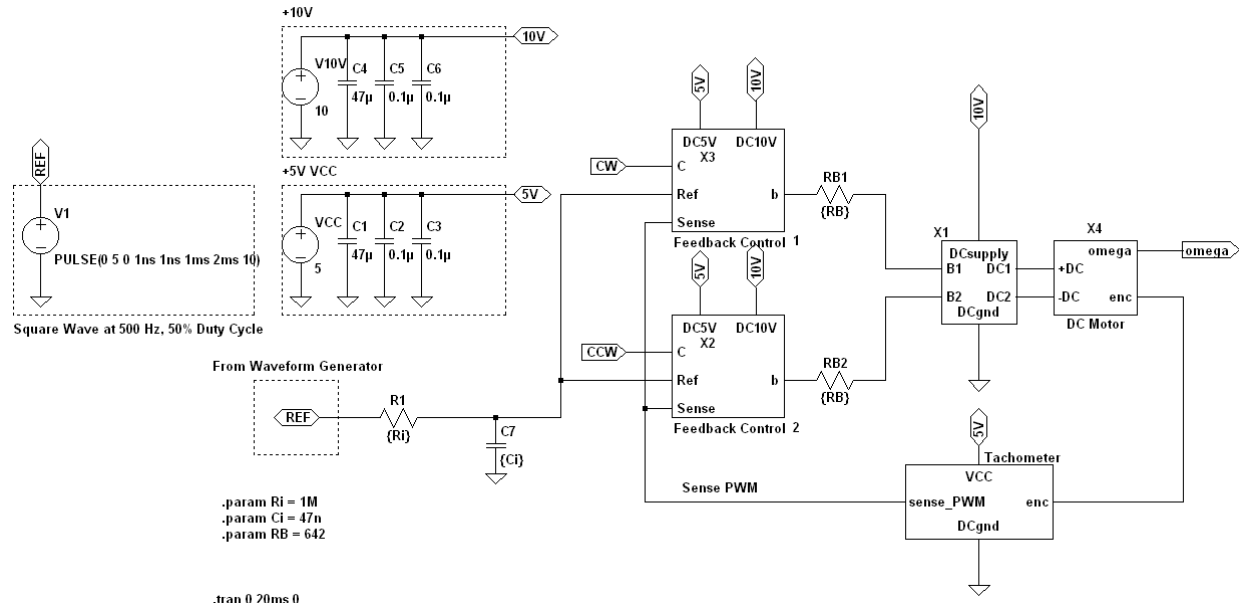


Figure 5: The Total Speed Control Schematic

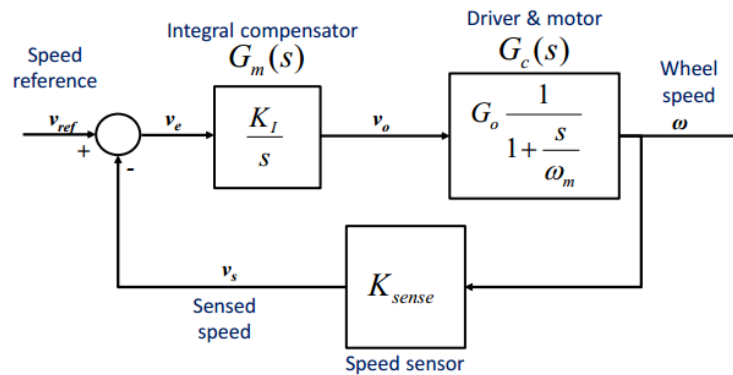


Figure 6: System Schematic of Circuit

3 Integral Compensator

We built the Integral compensator, shown below in Figure 7.

We used the original low-pass filter components R_3 and C_3 as an initial set of starting values. However, the integral compensator is not an isolated part of the circuit; its output in turn will affect its own input. Using a function generator for V_{ref} with a square wave amplitude $0 - 5[V]$, with a frequency of $1[kHz]$, we varied the duty cycle and found that the wheel's speed was proportional to the percent time on for V_{ref} . Ideally, the wheel speed would reach the highest speed possible. However, because $t_{on} = \frac{3}{4f_{enc}}$, the highest PWM duty cycle is limited, meaning the final speed is some fraction of the maximum encoder frequency f_{enc} , which was measured previously as approximately $1.2[kHz]$.

The transfer function for the integral compensator $G_m(s)$ is derived below:

$$\begin{aligned}
 v_n &= v_p \\
 i_n &= i_p \approx 0 \\
 \frac{v_s - v_n}{R_I} - \frac{v_n - v_o}{\frac{1}{sC_I}} &= 0 \\
 \frac{v_{ref} - v_p}{R_I} - \frac{v_p}{\frac{1}{sC_I}} &= 0 \\
 v_o(s) &= \frac{v_{ref} - v_s}{sR_IC_I} \\
 K_I &= \frac{1}{R_IC_I} \\
 G_m(s) &= \frac{K_I(v_{ref} - v_s)}{s}
 \end{aligned}$$

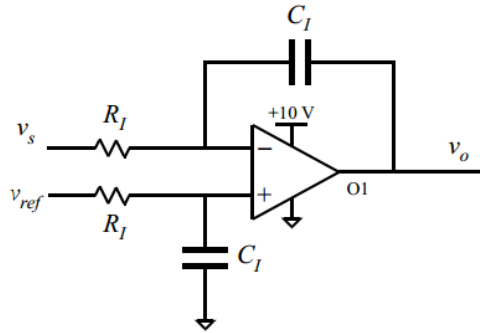


Figure 7: Integral Compensator

4 Transient Response

The integral compensator, however, would not necessarily work with the values used for R_3 and C_3 used in the Low-Pass Filter of Lab 2. This is because the feedback system gives rise to a Second- Order system. Our next task was to find a better value for R_I and C_I . As seen in Figure 8, we had to first seek out values for C_I and R_I that would not violate parameters from previous labs, but also be critically damped, that is, have a $\zeta = 1$. In order to calculate this, we have to find $G(s)$ and then set up the expression to solve for ζ seen in Equation (8).


$$\frac{v_o(s)}{v_{ref}(s)} = G(s) = \frac{H_0}{1 + 2\zeta \frac{s}{\omega_0} + (\frac{s}{\omega_0})^2} \quad (8)$$

Also, given in the lectures, we have important values K_{sense} and ω_0 .

$$K_{sense} = \frac{V_{smax} * 12 * 64}{2\pi f_{encmax}}$$

$$\omega_0 = \sqrt{\frac{kK_I K_{sense}}{JR_I}}$$

$$\zeta = \frac{1}{2}k\sqrt{\frac{k}{K_I K_{sense} JR_I}}$$

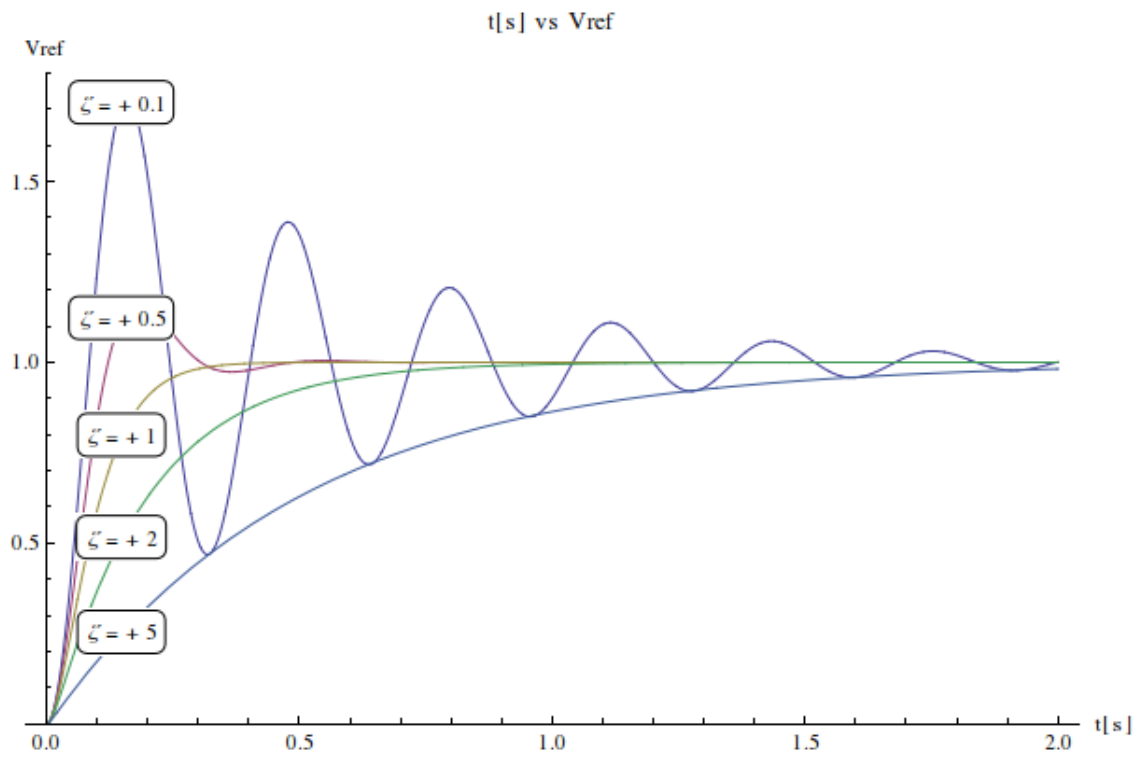Figure 8: Transients and ζ

4.1 w vs V_{ref} for CW and CCW Operation**4.2 K_{sense}** **4.3 Derivation of Closed-Loop Transfer Function $G(s)$** **4.4 Poles of $G(s)$** **4.5 Step Response Evaluation****4.6 Response time of the Speed Controller****5 Stop and Go Control**

Using a PMOS transistor, with the Source tied to 5[V], the Drain to the point after the R_I on the negative terminal on the op amp